

BJT distribuzione portatori minoritari


 


Fig. 7 Minority carrier distributions in various regions of a $p-n-p$ transistor under active mode of operation.

Distribuzione portatori minoritari

 



 
 


Figura 4.4: Configurazioni di utilizzo del transistor bjt: a) base comune; b) emettitore comune; c) collettore comune.

Base Comune


 


(b) Emitter characteristics

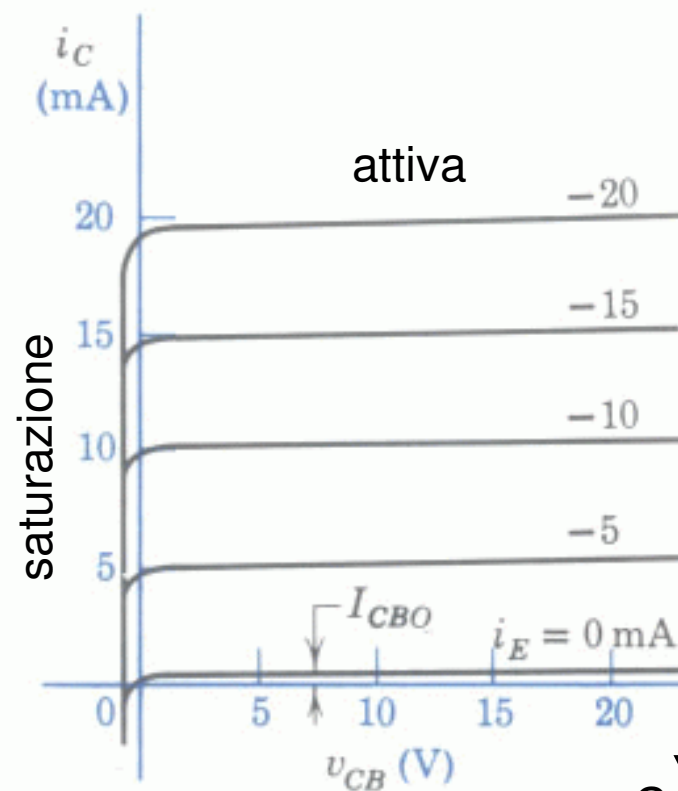


(c) Collector characteristics

Emettitore Comune

  


(a) Base characteristics

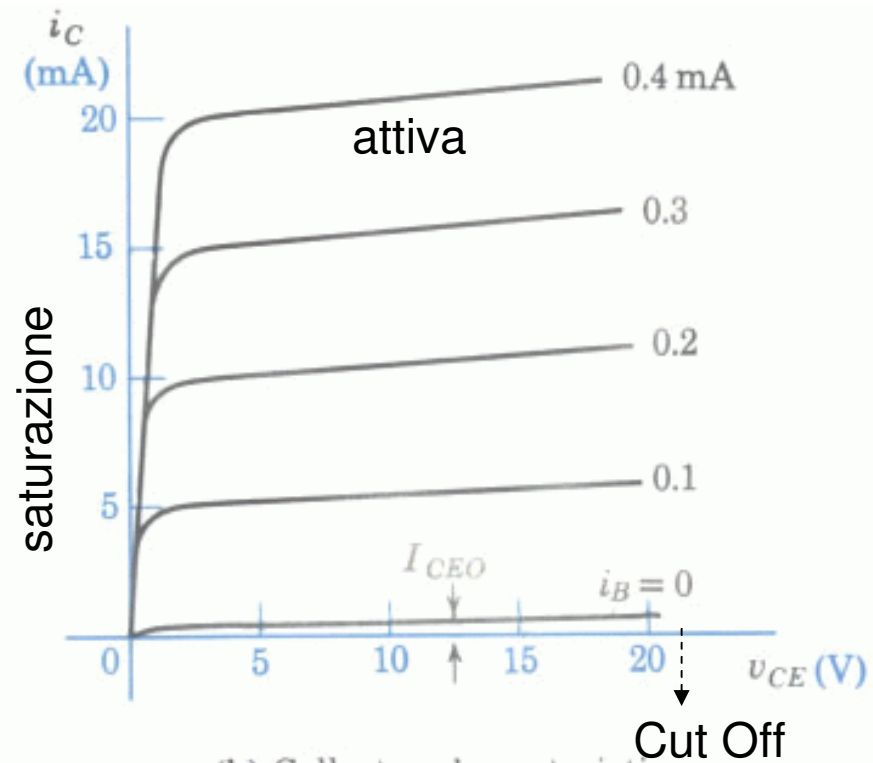


(b) Collector characteristics

Amplificatore di tensione e/o corrente

 

Emettitore Comune

 


$$\Delta V_{BE} = 0.07V$$


$$\Delta V_{CE} = 5V$$

$$\Delta i_B = 0.1mA$$

$$\Delta i_C = 5mA$$

 


(a) Base characteristics

 

(b) Collector characteristics

Base Comune

 


$$\Delta V_{EB} = 0.1V$$


$$\Delta V_{CB} = 11V$$

$$\Delta i_E = 10mA$$


$$\Delta i_C = 10mA$$

 


(b) Emitter characteristics

 

(c) Collector characteristics

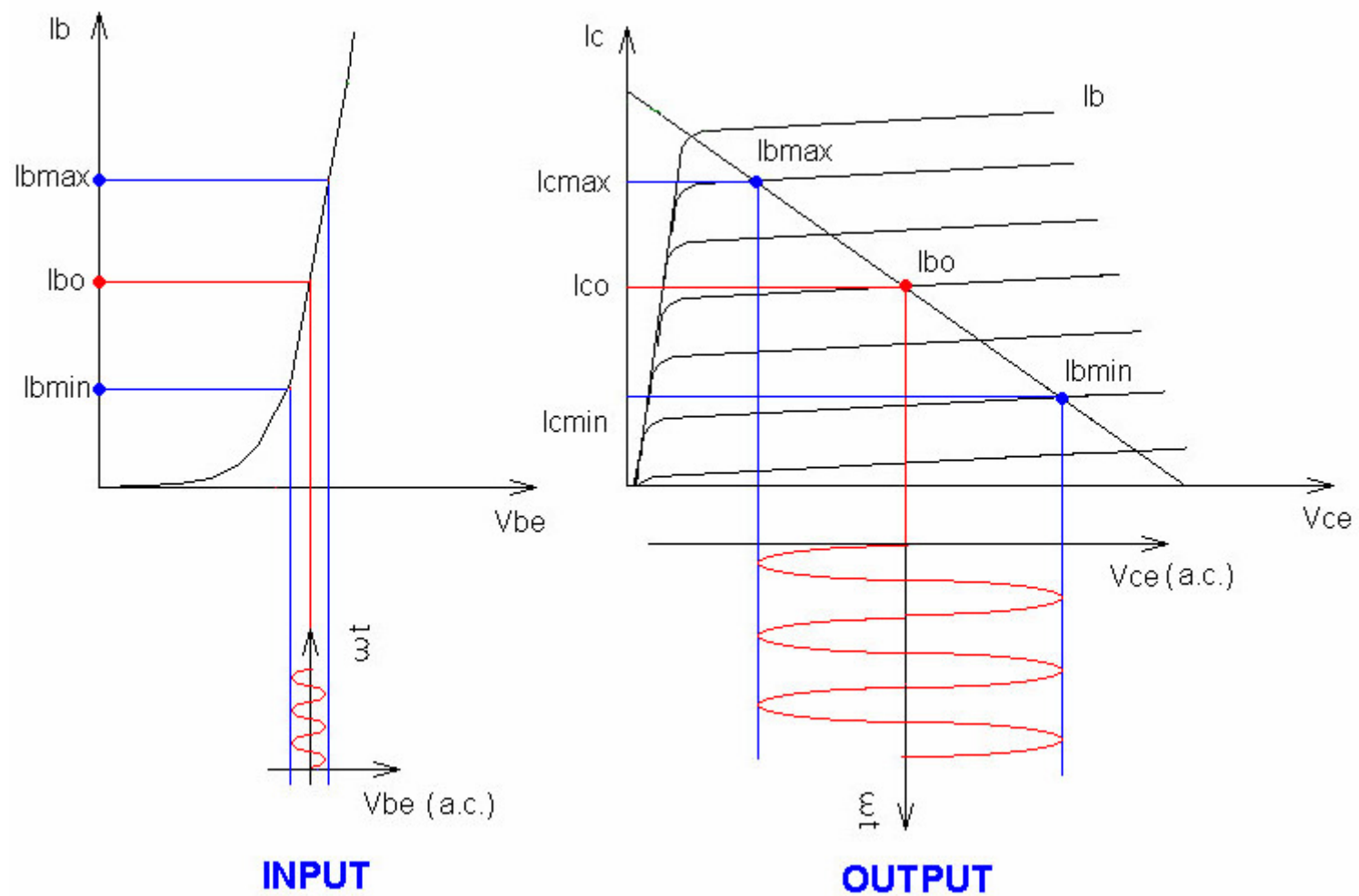



Collettore Comune

 


$$\Delta i_B = 0.1 \text{ mA}$$

$$\Delta V_{BE} = 0.07 \text{ V}$$



$$\Delta i_E = 5 \text{ mA}$$

  


Switch

 

OFF

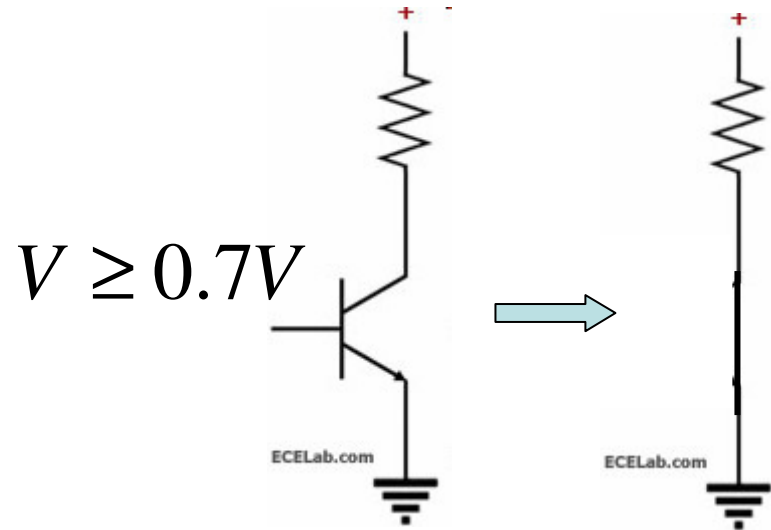 

ON

 

JFET

 
 


Fig. 10.23. Perspective view of the active part of a junction field-effect transistor. (After Millman and Halkias, "Integrated Electronics: Analog and Digital Circuits and Systems," McGraw-Hill, 1972.)

JFET

 


Fig. 10.24. Schematic view of the same transistor showing the doping of various regions. (After Leturcq and Rey, "Physique des Composants Actifs à Semi-conducteurs," Dunod, 1978.)

$$V_G \leq 0 \quad V_D \geq 0$$

JFET

 


Fig. 10.26. Depleted regions and the conducting channel in a polarized JFET.


 


Fig. 10 Variation of depletion layer width and output characteristics of a JFET under various biasing conditions. (a) $V_G = 0$ and small V_D . (b) $V_G = 0$ and at pinch-off. (c) $V_G = 0$ and post pinch-off ($V_D > V_{Dsat}$). (d) $V_G = -1V$ and small V_D .

JFET: pinch off

 

JFET: caratteristiche statiche

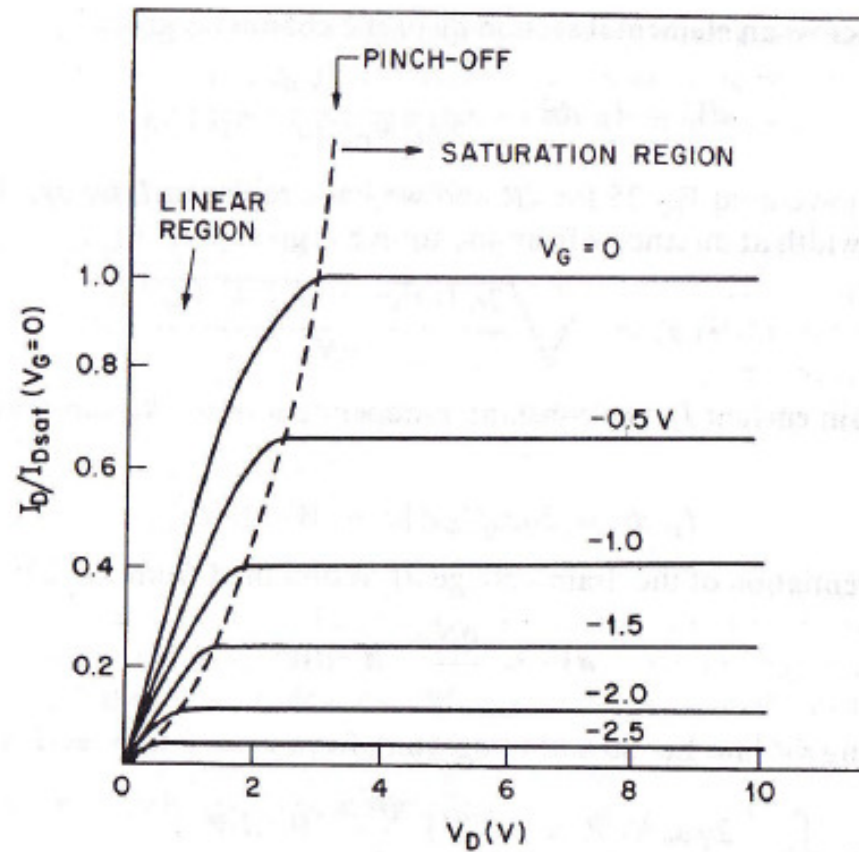


Fig. 12 Normalized ideal current-voltage characteristics with $V_p = 3.2$ V.

JFET: confronto modello dati

$$g_D = \frac{\partial I_D}{\partial V_D} \text{ Conduttanza}$$

$$g_m = \frac{\partial I_D}{\partial V_G} \text{ Transconduttanza}$$

 


Fig. 13 Normalized drain conductance in the linear region and normalized transconductance in the saturation region versus normalized gate voltage. Solid line is for the ideal case; dotted line is for a practical device having series resistances.

JFET: comportamento dinamico

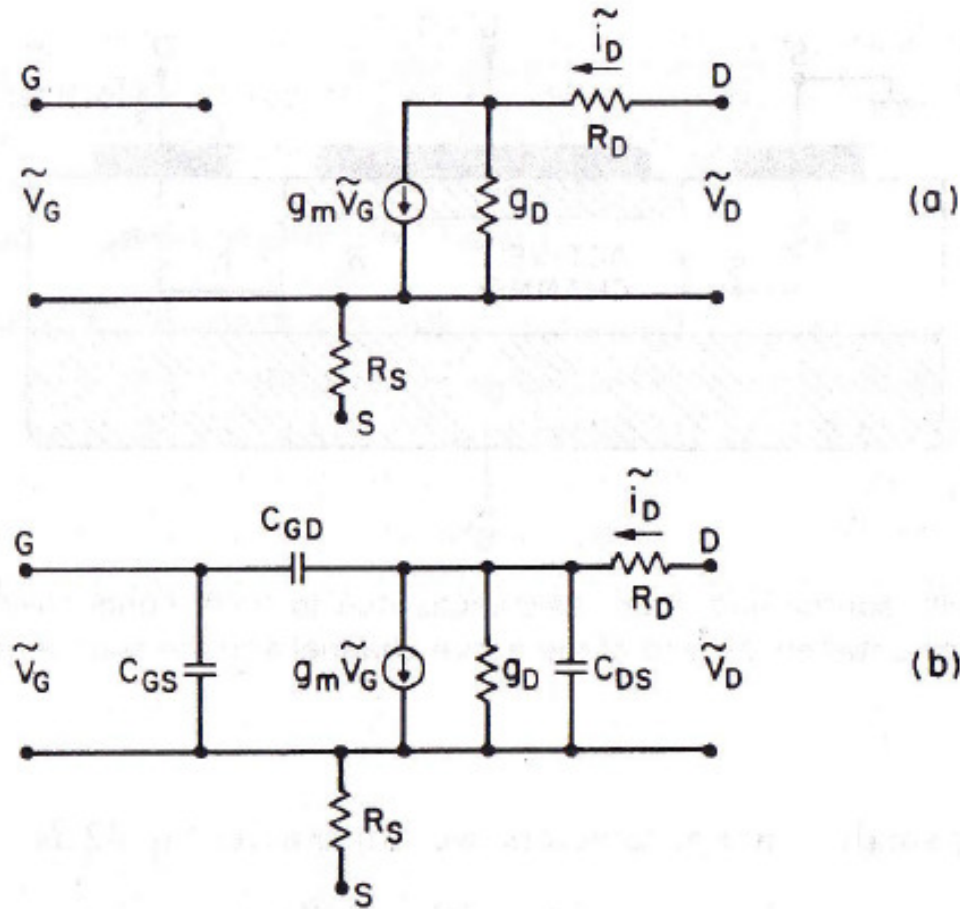


Fig. 15 (a) Low-frequency, small-signal equivalent circuit of the JFET. (b) High-frequency, small-signal equivalent circuit of the JFET.